

# Assignment 2 Part 2

## Multiplexer and Demultiplexer

A multiplexer is a circuit that accept many input but give only one output. A demultiplexer function exactly in the reverse of a multiplexer, that is a demultiplexer accepts only one input and gives many outputs. Generally multiplexer and demultiplexer are used together, because of the communication systems are bi directional.

### Multiplexer:


Multiplexer means many into one. A multiplexer is a circuit used to select and route any one of the several input signals to a signal output. An simple example of an non electronic circuit of a multiplexer is a single pole multiposition switch.

Multiposition switches are widely used in many electronics circuits. However circuits that operate at high speed require the multiplexer to be automatically selected. A mechanical switch cannot perform this task satisfactorily. Therefore, multiplexer used to perform high speed switching are constructed of electronic components.

Multiplexer handle two type of data that is analog and digital. For analog application, multiplexer are built of relays and transistor switches. For digital application, they are built from standard logic gates.

The multiplexer used for digital applications, also called digital multiplexer, is a circuit with many input but only one output. By applying control signals, we can steer any input to the output. Few types of multiplexer are 2-to-1, 4-to-1, 8-to-1, 16-to-1 multiplexer.

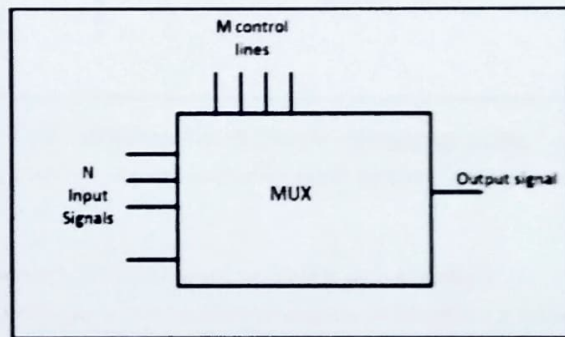Following figure shows the general idea of a multiplexer with n input signal, m control signals and one output signal.




Multiplexer Pin Diagram
 
### Understanding 4-to-1 Multiplexer:

The 4-to-1 multiplexer has 4 input bit, 2 control bits, and 1 output bit. The four input bits are  $D_0, D_1, D_2$  and  $D_3$ . only one of this is transmitted to the output  $y$ . The output depends on the value of  $AB$  which is the control input. The control input determines which of the input data bit is transmitted to the output.

For instance, as shown in fig. when  $AB = 00$ , the upper AND gate is enabled while all other AND gates are disabled. Therefore, data bit  $D_0$  is transmitted to the output, giving  $Y = D_0$ .



4 to 1 Multiplexer Circuit Diagram – [ElectronicsHub.Org](http://ElectronicsHub.Org)

If the control input is changed to  $AB = 11$ , all gates are disabled except the bottom AND gate. In this case, D3 is transmitted to the output and  $Y = D3$ .

- An example of 4-to-1 multiplexer is IC 74153 in which the output is same as the input.
- Another example of 4-to-1 multiplexer is 45352 in which the output is the compliment of the input.
- Example of 16-to-1 line multiplexer is IC74150.

### ***Applications of Multiplexer:***

Multiplexer are used in various fields where multiple data need to be transmitted using a single line. Following are some of the applications of multiplexers -


1. **Communication system** – Communication system is a set of system that enable communication like transmission system, relay and tributary station, and communication network. The efficiency of communication system can be increased considerably using multiplexer. Multiplexer allow the process of transmitting different type of data such as audio, video at the same time using a single transmission line.

2. **Telephone network** – In telephone network, multiple audio signals are integrated on a single line for transmission with the help of multiplexers. In this way, multiple audio signals can be isolated and eventually, the desired audio signals reach the intended recipients.
3. **Computer memory** - Multiplexers are used to implement huge amount of memory into the computer, at the same time reduces the number of copper lines required to connect the memory to other parts of the computer circuit.
4. **Transmission from the computer system of a satellite** – Multiplexer can be used for the transmission of data signals from the computer system of a satellite or spacecraft to the ground system using the GPS (Global Positioning System) satellites.
 
## Demultiplexer:

Demultiplexer means one to many. A demultiplexer is a circuit with one input and many output. By applying control signal, we can steer any input to the output. Few types of demultiplexer are 1-to-2, 1-to-4, 1-to-8 and 1-to-16 demultiplexer.


Following figure illustrate the general idea of a demultiplexer with 1 input signal,  $m$  control signals, and  $n$  output signals.



Demultiplexer Pin Diagram
 
## Understanding 1- to-4 Demultiplexer:

The 1-to-4 demultiplexer has 1 input bit, 2 control bit, and 4 output bits. An example of 1-to-4 demultiplexer is IC 74155. The 1-to-4 demultiplexer is shown in figure below-



1 to 4 Demultiplexer Circuit Diagram – [ElectronicsHub.Org](http://ElectronicsHub.Org)

The input bit is labelled as Data D. This data bit is transmitted to the data bit of the output lines. This depends on the value of AB, the control input

When  $AB = 01$ , the upper second AND gate is enabled while other AND gates are disabled. Therefore, only data bit D is transmitted to the output, giving  $Y1 = \text{Data}$

If D is low, Y1 is low. If D is high, Y1 is high. The value of Y1 depends upon the value of D. All other outputs are in low state

If the control input is changed to  $AB = 10$ , all the gates are disabled except the third AND gate from the top. Then, D is transmitted only to the Y2 output, and  $Y2 = \text{Data}$

Example of 1-to-16 demultiplexer is IC 74154 it has 1 input bit, 4 control bits and 16 output bit

## ***Applications of Demultiplexer:***

1. Demultiplexer is used to connect a single source to multiple destinations. The main application area of demultiplexer is communication system where multiplexer are used. Most of the communication system are bidirectional i.e. they function in both ways (transmitting and receiving signals). Hence, for most of the applications, the multiplexer and demultiplexer work in sync. Demultiplexer are also used for reconstruction of parallel data and ALU circuits.
2. **Communication System** - Communication system use multiplexer to carry multiple data like audio, video and other form of data using a single line for transmission. This process make the transmission easier. The demultiplexer receive the output signals of the multiplexer and converts them back to the original form of the data at the receiving end. The multiplexer and demultiplexer work together to carry out the process of transmission and reception of data in communication system.
3. **ALU (Arithmetic Logic Unit)** – In an ALU circuit, the output of ALU can be stored in multiple registers or storage units with the help of demultiplexer. The output of ALU is fed as the data input to the demultiplexer. Each output of demultiplexer is connected to multiple register which can be stored in the registers.
4. **Serial to parallel converter** - A serial to parallel converter is used for reconstructing parallel data from incoming serial data stream. In this technique, serial data from the incoming serial data stream is given as data input to the demultiplexer at the regular intervals. A counter is attach to the control input of the demultiplexer. This counter directs the data signal to the output of the demultiplexer where these data signals are stored. When all data signals have been stored, the output of the demultiplexer can be retrieved and read out in parallel.


Source: <http://www.electronicshub.org/multiplexer-and-demultiplexer/>

**Multiplexer** is a combinational circuit that has maximum of  $2^n$  data inputs, 'n' selection lines and single output line. One of these data inputs will be connected to the output based on the values of selection lines.

Since there are 'n' selection lines, there will be  $2^n$  possible combinations of zeros and ones. So, each combination will select only one data input. Multiplexer is also called as **Mux**.
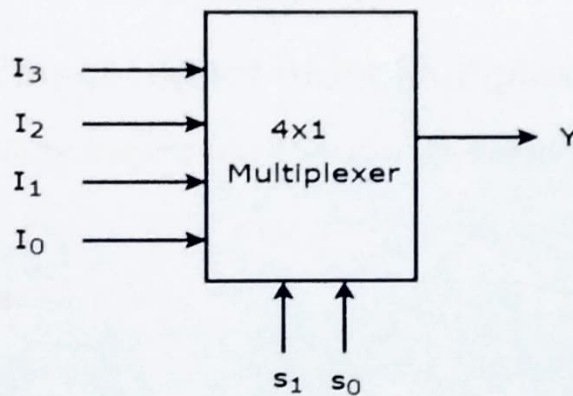
## 4x1 Multiplexer

4x1 Multiplexer has four data inputs  $I_3, I_2, I_1$  &  $I_0$ , two selection lines  $s_1$  &  $s_0$  and one output Y. The **block diagram** of 4x1 Multiplexer is shown in the following figure.




One of these 4 inputs will be connected to the output based on the combination of inputs present at these two selection lines. **Truth table** of 4x1 Multiplexer is shown below.

| Selection Lines |       | Output |
|-----------------|-------|--------|
| $S_1$           | $S_0$ | Y      |
| 0               | 0     | $I_0$  |
| 0               | 1     | $I_1$  |
| 1               | 0     | $I_2$  |
| 1               | 1     | $I_3$  |

From Truth table, we can directly write the **Boolean function** for output, Y as

$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

 We can implement this Boolean function using Inverters, AND gates & OR gate. The **circuit diagram** of 4x1 multiplexer is shown in the following figure.



We can easily understand the operation of the above circuit. Similarly, you can implement 8x1 Multiplexer and 16x1 multiplexer by following the same procedure.

## Implementation of Higher-order Multiplexers.

Now, let us implement the following two higher-order Multiplexers using lower-order Multiplexers.

- 8x1 Multiplexer
- 16x1 Multiplexer

### 8x1 Multiplexer


In this section, let us implement 8x1 Multiplexer using 4x1 Multiplexers and 2x1 Multiplexer. We know that 4x1 Multiplexer has 4 data inputs, 2 selection lines and one output. Whereas, 8x1 Multiplexer has 8 data inputs, 3 selection lines and one output.

So, we require two **4x1 Multiplexers** in first stage in order to get the 8 data inputs. Since, each 4x1 Multiplexer produces one output, we require a **2x1 Multiplexer** in second stage by considering the outputs of first stage as inputs and to produce the final output.

Let the 8x1 Multiplexer has eight data inputs  $I_7$  to  $I_0$ , three selection lines  $s_2$ ,  $s_1$  &  $s_0$  and one output  $Y$ . The **Truth table** of 8x1 Multiplexer is shown below.

| Selection Inputs |       |       | Output |
|------------------|-------|-------|--------|
| $S_2$            | $S_1$ | $S_0$ | $Y$    |
| 0                | 0     | 0     | $I_0$  |
| 0                | 0     | 1     | $I_1$  |
| 0                | 1     | 0     | $I_2$  |
| 0                | 1     | 1     | $I_3$  |
| 1                | 0     | 0     | $I_4$  |
| 1                | 0     | 1     | $I_5$  |
| 1                | 1     | 0     | $I_6$  |
| 1                | 1     | 1     | $I_7$  |

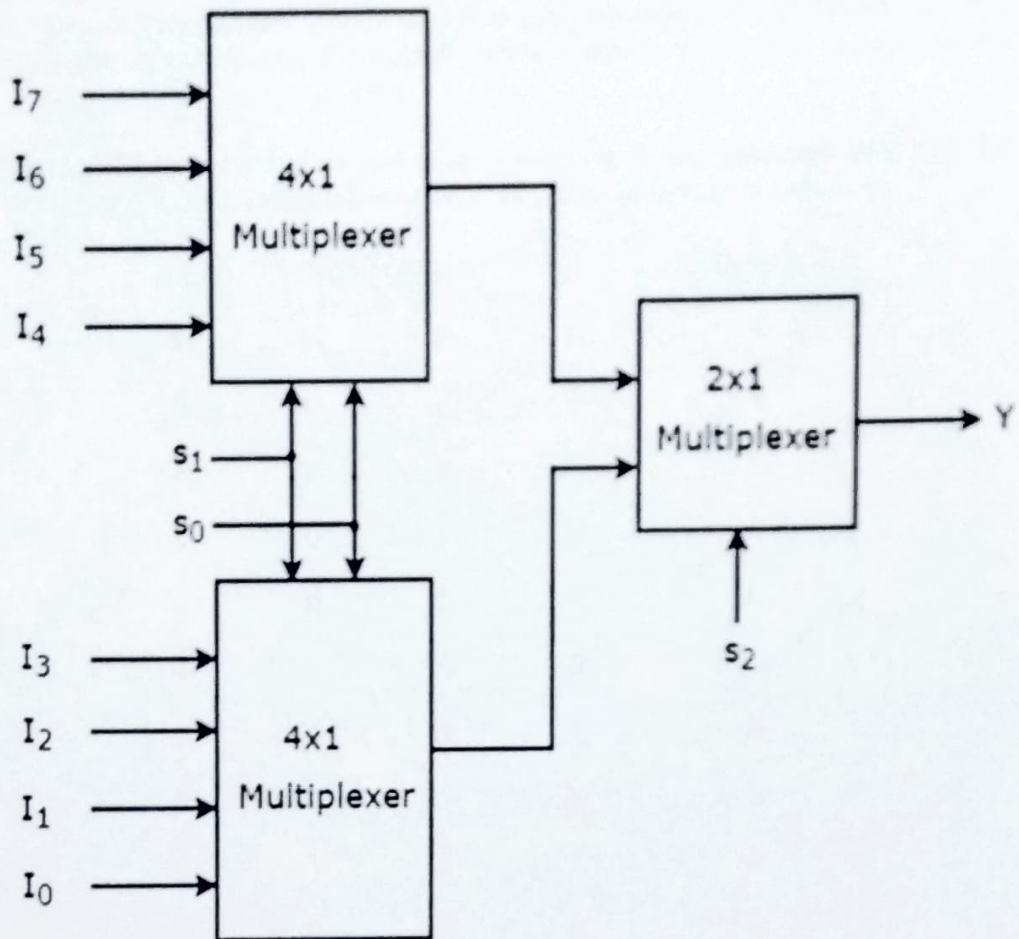We can implement 8x1 Multiplexer using lower order Multiplexers easily by considering the above Truth table. The block diagram of 8x1 Multiplexer is shown in the following figure.



The same **selection lines,  $s_1$  &  $s_0$**  are applied to both 4x1 Multiplexers. The data inputs of upper 4x1 Multiplexer are  $I_7$  to  $I_4$ , and the data inputs of lower 4x1 Multiplexer are  $I_3$  to  $I_0$ . Therefore, each 4x1 Multiplexer produces an output based on the values of selection lines,  $s_1$  &  $s_0$ .

The outputs of first stage 4x1 Multiplexers are applied as inputs of 2x1 Multiplexer that is present in second stage. The other **selection line,  $s_2$**  is applied to 2x1 Multiplexer.

- If  $s_2$  is zero, then the output of 2x1 Multiplexer will be one of the 4 inputs  $I_3$  to  $I_0$ , based on the values of selection lines  $s_1$  &  $s_0$ .
- If  $s_2$  is one, then the output of 2x1 Multiplexer will be one of the 4 inputs  $I_7$  to  $I_4$ , based on the values of selection lines  $s_1$  &  $s_0$ .

Therefore, the overall combination of two 4x1 Multiplexers and one 2x1 Multiplexer performs as one 8x1 Multiplexer.

### 16x1 Multiplexer

In this section, let us implement 16x1 Multiplexer using 8x1 Multiplexers and 2x1 Multiplexer. We know that 8x1 Multiplexer has 8 data inputs, 3 selection lines and




one output. Whereas, 16x1 Multiplexer has 16 data inputs, 4 selection lines and one output.

So, we require two **8x1 Multiplexers** in first stage in order to get the 16 data inputs. Since, each 8x1 Multiplexer produces one output, we require a 2x1 Multiplexer in second stage by considering the outputs of first stage as inputs and to produce the final output.

Let the 16x1 Multiplexer has sixteen data inputs  $I_{15}$  to  $I_0$ , four selection lines  $s_3$  to  $s_0$  and one output  $Y$ . The **Truth table** of 16x1 Multiplexer is shown below.

| Selection Inputs |       |       |       | Output   |
|------------------|-------|-------|-------|----------|
| $S_3$            | $S_2$ | $S_1$ | $S_0$ | $Y$      |
| 0                | 0     | 0     | 0     | $I_0$    |
| 0                | 0     | 0     | 1     | $I_1$    |
| 0                | 0     | 1     | 0     | $I_2$    |
| 0                | 0     | 1     | 1     | $I_3$    |
| 0                | 1     | 0     | 0     | $I_4$    |
| 0                | 1     | 0     | 1     | $I_5$    |
| 0                | 1     | 1     | 0     | $I_6$    |
| 0                | 1     | 1     | 1     | $I_7$    |
| 1                | 0     | 0     | 0     | $I_8$    |
| 1                | 0     | 0     | 1     | $I_9$    |
| 1                | 0     | 1     | 0     | $I_{10}$ |
| 1                | 0     | 1     | 1     | $I_{11}$ |
| 1                | 1     | 0     | 0     | $I_{12}$ |
| 1                | 1     | 0     | 1     | $I_{13}$ |
| 1                | 1     | 1     | 0     | $I_{14}$ |
| 1                | 1     | 1     | 1     | $I_{15}$ |

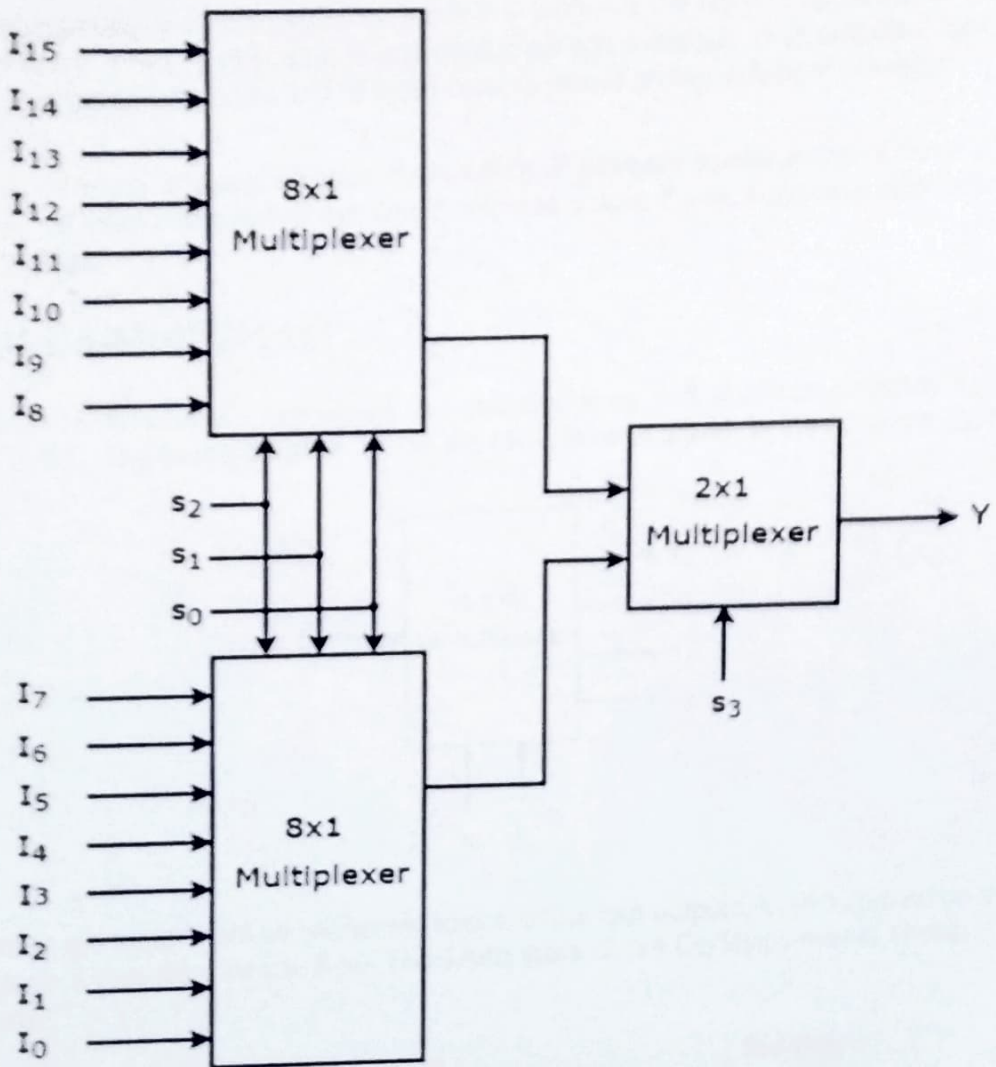We can implement 16x1 Multiplexer using lower order Multiplexers easily by considering the above Truth table. The **block diagram** of 16x1 Multiplexer is shown in the following figure.



The same selection lines,  $s_2$ ,  $s_1$  &  $s_0$  are applied to both 8x1 Multiplexers. The data inputs of upper 8x1 Multiplexer are  $I_{15}$  to  $I_8$  and the data inputs of lower 8x1 Multiplexer are  $I_7$  to  $I_0$ . Therefore, each 8x1 Multiplexer produces an output based on the values of selection lines,  $s_2$ ,  $s_1$  &  $s_0$ .

The outputs of first stage 8x1 Multiplexers are applied as inputs of 2x1 Multiplexer that is present in second stage. The other selection line,  $s_3$  is applied to 2x1 Multiplexer.

- If  $s_3$  is zero, then the output of 2x1 Multiplexer will be one of the 8 inputs  $I_7$  to  $I_0$  based on the values of selection lines  $s_2$ ,  $s_1$  &  $s_0$ .
- If  $s_3$  is one, then the output of 2x1 Multiplexer will be one of the 8 inputs  $I_{15}$  to  $I_8$  based on the values of selection lines  $s_2$ ,  $s_1$  &  $s_0$ .


Therefore, the overall combination of two 8x1 Multiplexers and one 2x1 Multiplexer performs as one 16x1 Multiplexer.

**De-Multiplexer** is a combinational circuit that performs the reverse operation of Multiplexer. It has single input, 'n' selection lines and maximum of  $2^n$  outputs. The input will be connected to one of these outputs based on the values of selection lines.

Since there are 'n' selection lines, there will be  $2^n$  possible combinations of zeros and ones. So, each combination can select only one output. De-Multiplexer is also called as **De-Mux**.
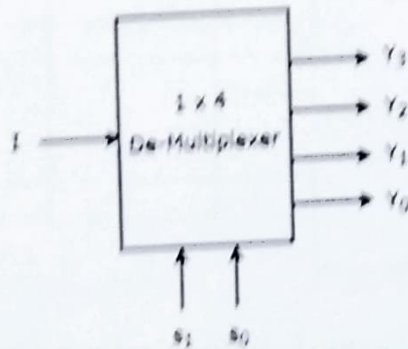
## 1x4 De-Multiplexer

1x4 De-Multiplexer has one input I, two selection lines,  $s_1$  &  $s_0$  and four outputs  $Y_3$ ,  $Y_2$ ,  $Y_1$ , &  $Y_0$ . The **block diagram** of 1x4 De-Multiplexer is shown in the following figure.



The single input 'I' will be connected to one of the four outputs,  $Y_3$  to  $Y_0$  based on the values of selection lines  $s_1$  &  $s_0$ . The **Truth table** of 1x4 De-Multiplexer is shown below.

| Selection Inputs |       | Outputs |       |       |       |
|------------------|-------|---------|-------|-------|-------|
| $s_1$            | $s_0$ | $Y_3$   | $Y_2$ | $Y_1$ | $Y_0$ |
| 0                | 0     | 0       | 0     | 0     | 1     |
| 0                | 1     | 0       | 0     | 1     | 0     |
| 1                | 0     | 0       | 1     | 0     | 0     |
| 1                | 1     | 1       | 0     | 0     | 0     |


From the above Truth table, we can directly write the **Boolean functions** for each output as

$$Y_3 = s_1 s_0 / Y_3 = s_1 s_0 1$$


$$Y_2 = s_1 \bar{s}_0 / Y_2 = s_1 \bar{s}_0 1$$

$$Y_1 = \bar{s}_1 s_0 / Y_1 = \bar{s}_1 s_0 1$$
 
$$Y_0 = \bar{s}_1 \bar{s}_0 / Y_0 = \bar{s}_1 \bar{s}_0 1$$



 We can implement these Boolean functions using Inverters & 3-input AND gates. The **circuit diagram** of 1x4 De-Multiplexer is shown in the following figure.



We can easily understand the operation of the above circuit. Similarly, you can implement 1x8 De-Multiplexer and 1x16 De-Multiplexer by following the same procedure.

## Implementation of Higher-order De-Multiplexers

Now, let us implement the following two higher-order De-Multiplexers using lower-order De-Multiplexers.

- 1x8 De-Multiplexer
- 1x16 De-Multiplexer

### 1x8 De-Multiplexer


In this section, let us implement 1x8 De-Multiplexer using 1x4 De-Multiplexers and 1x2 De-Multiplexer. We know that 1x4 De-Multiplexer has single input, two selection lines and four outputs. Whereas, 1x8 De-Multiplexer has single input, three selection lines and eight outputs.

So, we require two **1x4 De-Multiplexers** in second stage in order to get the final eight outputs. Since, the number of inputs in second stage is two, we require **1x2 De-Multiplexer** in first stage so that the outputs of first stage will be the inputs of second stage. Input of this 1x2 De-Multiplexer will be the overall input of 1x8 De-Multiplexer.

Let the 1x8 De-Multiplexer has one input  $I$ , three selection lines  $s_2$ ,  $s_1$  &  $s_0$  and outputs  $Y_7$  to  $Y_0$ . The **Truth table** of 1x8 De-Multiplexer is shown below.

| Selection Inputs |       |       | Outputs |       |       |       |       |       |       |       |
|------------------|-------|-------|---------|-------|-------|-------|-------|-------|-------|-------|
| $s_2$            | $s_1$ | $s_0$ | $Y_7$   | $Y_6$ | $Y_5$ | $Y_4$ | $Y_3$ | $Y_2$ | $Y_1$ | $Y_0$ |
| 0                | 0     | 0     | 0       | 0     | 0     | 0     | 0     | 0     | 0     | 1     |
| 0                | 0     | 1     | 0       | 0     | 0     | 0     | 0     | 0     | 1     | 0     |
| 0                | 1     | 0     | 0       | 0     | 0     | 0     | 0     | 1     | 0     | 0     |
| 0                | 1     | 1     | 0       | 0     | 0     | 0     | 1     | 0     | 0     | 0     |
| 1                | 0     | 0     | 0       | 0     | 0     | 1     | 0     | 0     | 0     | 0     |
| 1                | 0     | 1     | 0       | 0     | 1     | 0     | 0     | 0     | 0     | 0     |
| 1                | 1     | 0     | 0       | 1     | 0     | 0     | 0     | 0     | 0     | 0     |
| 1                | 1     | 1     | 1       | 0     | 0     | 0     | 0     | 0     | 0     | 0     |

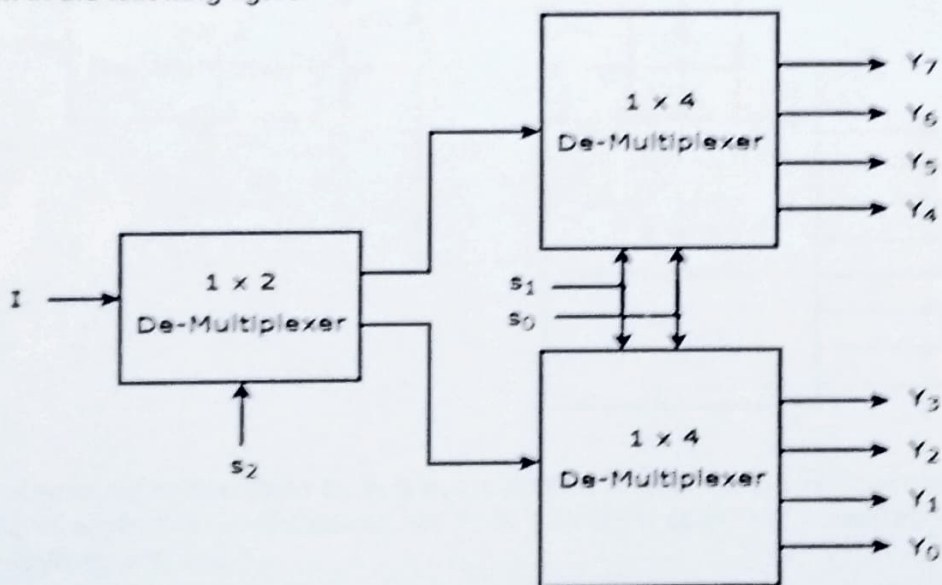We can implement 1x8 De-Multiplexer using lower order Multiplexers easily by considering the above Truth table. The block diagram of 1x8 De-Multiplexer is shown in the following figure.



The common selection lines,  $s_1$  &  $s_0$  are applied to both 1x4 De-Multiplexers. The outputs of upper 1x4 De-Multiplexer are  $Y_7$  to  $Y_4$ , and the outputs of lower 1x4 De-Multiplexer are  $Y_3$  to  $Y_0$ .


The other selection line,  $s_2$  is applied to 1x2 De-Multiplexer. If  $s_2$  is zero, then one of the four outputs of lower 1x4 De-Multiplexer will be equal to input,  $I$  based on the values of selection lines  $s_1$  &  $s_0$ . Similarly, if  $s_2$  is one, then one of the four outputs of upper 1x4 De-Multiplexer will be equal to input,  $I$  based on the values of selection lines  $s_1$  &  $s_0$ .

## 1x16 De-Multiplexer

In this section, let us implement 1x16 De-Multiplexer using 1x8 De-Multiplexers and 1x2 De-Multiplexer. We know that 1x8 De-Multiplexer has single input, three selection lines and eight outputs. Whereas, 1x16 De-Multiplexer has single input, four selection lines and sixteen outputs.

So, we require two 1x8 De-Multiplexers in second stage in order to get the final sixteen outputs. Since, the number of inputs in second stage is two, we require 1x2 De-Multiplexer in first stage so that the outputs of first stage will be the inputs of second stage. Input of this 1x2 De-Multiplexer will be the overall input of 1x16 De-Multiplexer.

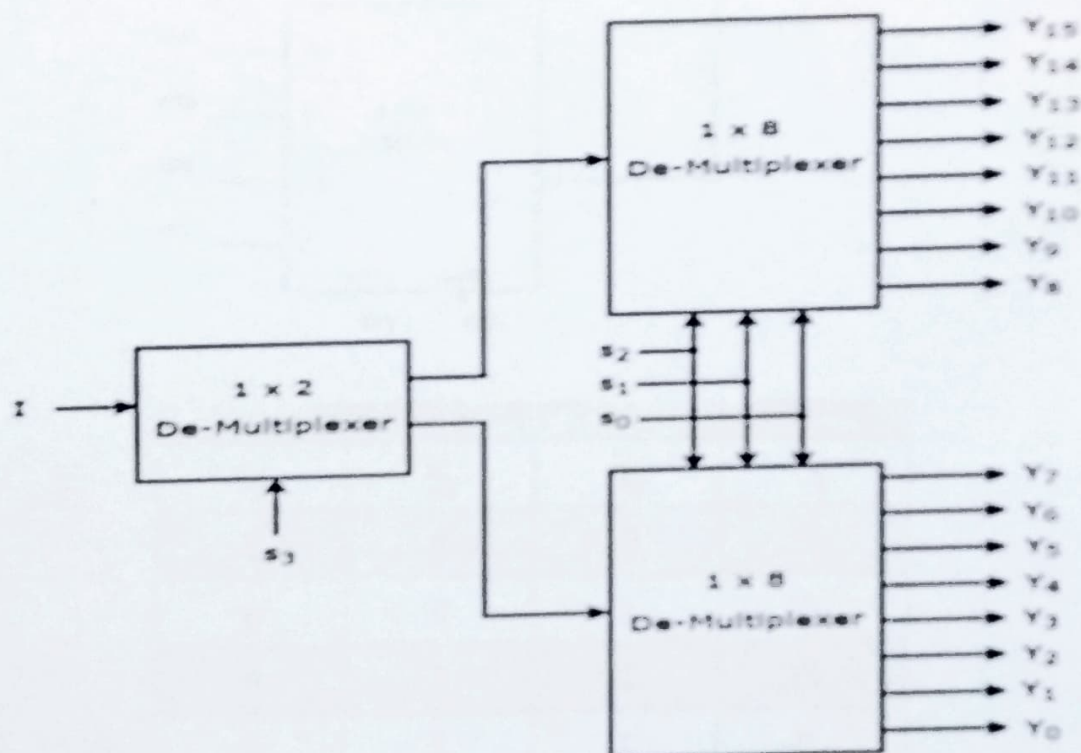
Let the 1x16 De-Multiplexer has one input  $I$ , four selection lines  $s_3, s_2, s_1$  &  $s_0$ , and outputs  $Y_{15}$  to  $Y_0$ . The block diagram of 1x16 De-Multiplexer using lower order Multiplexers is shown in the following figure.



The common selection lines  $s_2, s_1$  &  $s_0$  are applied to both 1x8 De-Multiplexers. The outputs of upper 1x8 De-Multiplexer are  $Y_{15}$  to  $Y_8$  and the outputs of lower 1x8 De-Multiplexer are  $Y_7$  to  $Y_0$ .

The other selection line,  $s_3$  is applied to 1x2 De-Multiplexer. If  $s_3$  is zero, then one of the eight outputs of lower 1x8 De-Multiplexer will be equal to input,  $I$  based on the values of selection lines  $s_2, s_1$  &  $s_0$ . Similarly, if  $s_3$  is one, then one of the 8 outputs of upper 1x8 De-Multiplexer will be equal to input,  $I$  based on the values of selection lines  $s_2, s_1$  &  $s_0$ .

# Multiplexer

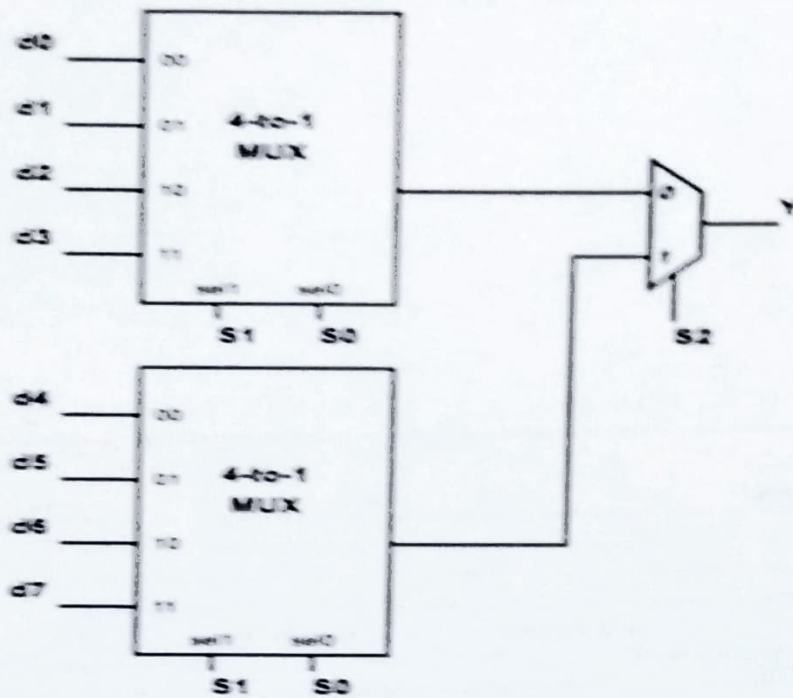

| Select Data Inputs |       |       | Output |
|--------------------|-------|-------|--------|
| $S_2$              | $S_1$ | $S_0$ | $Y$    |
| 0                  | 0     | 0     | $D_0$  |
| 0                  | 0     | 1     | $D_1$  |
| 0                  | 1     | 0     | $D_2$  |
| 0                  | 1     | 1     | $D_3$  |
| 1                  | 0     | 0     | $D_4$  |
| 1                  | 0     | 1     | $D_5$  |
| 1                  | 1     | 0     | $D_6$  |
| 1                  | 1     | 1     | $D_7$  |




## VHDL Code for a Multiplexer

```
Library ieee;
use ieee.std_logic_1164.all;

entity mux is
  port(S1,S0,D0,D1,D2,D3:in bit; Y:out bit);
end mux;

architecture data of mux is
begin
  Y<= (not S0 and not S1 and D0) or
      (S0 and not S1 and D1) or
      (not S0 and S1 and D2) or
      (S0 and S1 and D3);
end data;
```

### Waveforms

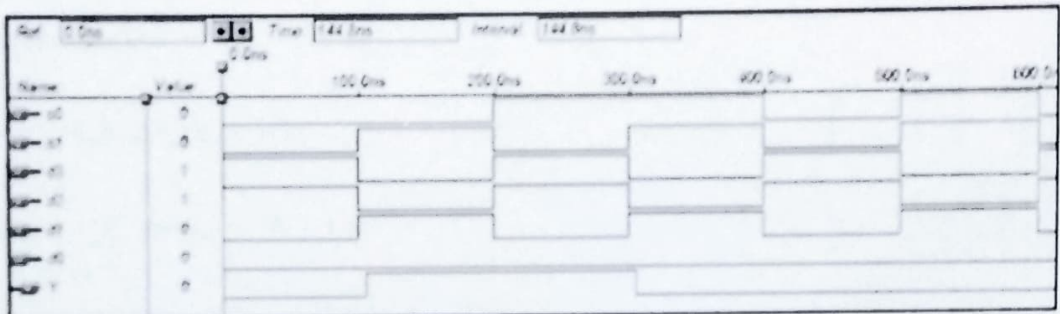


## VHDL Code for a Demultiplexer

```
Library ieee;
use ieee.std_logic_1164.all;

entity demux is
  port(S1,S0,D:in bit; Y0,Y1,Y2,Y3:out bit);
end demux;

architecture data of demux is
begin
  Y0<= ((Not S0) and (Not S1) and D);
  Y1<= ((Not S0) and S1 and D);
  Y2<= (S0 and (Not S1) and D);
  Y3<= (S0 and S1 and D);
end data;
```

### Waveforms

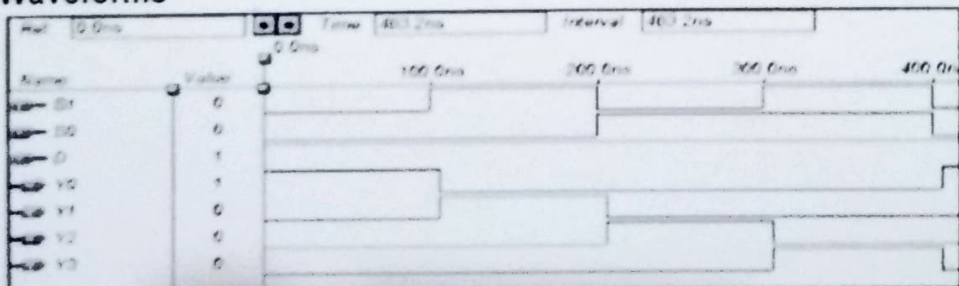

## VIEW SOURCE

## CODE


```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3
4 entity mux_4to1 is
5   port(
6
7     A,B,C,D : in STD_LOGIC;
8     S0,S1: in STD_LOGIC;
9     Z: out STD_LOGIC
10  );
11 end mux_4to1;
12
13 architecture bhv of mux_4to1 is
14 begin
15   process (A,B,C,D,S0,S1) is
16   begin
17     if (S0 = '0' and S1 = '0') then
18       Z <= A;
19     elsif (S0 = '1' and S1 = '0') then
20       Z <= B;
21     elsif (S0 = '0' and S1 = '1') then
22       Z <= C;
23     else
24       Z <= D;
25     end if;
26
27   end process;
28 end bhv;

```

Truth table

| S <sub>1</sub> | S <sub>0</sub> | output |
|----------------|----------------|--------|
| 0              | 0              | A      |
| 0              | 1              | B      |
| 1              | 0              | C      |
| 1              | 1              | D      |

 

view sourceprint?


```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3
4 entity demux_1to4 is
5 port(
6
7 F : in STD_LOGIC;
8 S0,S1: in STD_LOGIC;
9 A,B,C,D: out STD_LOGIC
10 );
11 end demux_1to4;
12
13 architecture bhv of demux_1to4 is
14 begin
15 process (F,S0,S1) is
16 begin
17 if (S0 = '0' and S1 = '0') then
18 A <= F;
19 elsif (S0 = '1' and S1 = '0') then
20 B <= F;
21 elsif (S0 = '0' and S1 = '1') then
22 C <= F;
23 else
24 D <= F;
25 end if;
26
27 end process;
28 end bhv;

```

Truth table

| Input | select line |    | output |   |   |   |
|-------|-------------|----|--------|---|---|---|
| F     | S1          | S0 | D      | C | B | A |
| 1     | 0           | 0  | 0      | 0 | 0 | 1 |
| 1     | 0           | 1  | 0      | 0 | 1 | 0 |
| 1     | 1           | 0  | 0      | 1 | 0 | 0 |
| 1     | 1           | 1  | 1      | 0 | 0 | 0 |
| 0     | X           | X  | 0      | 0 | 0 | 0 |

 

## STD\_LOGIC

### entity

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity mux4\_1 is

port(

A,B,C,D : in STD\_LOGIC;

S0,S1 : in STD\_LOGIC;

Z : out STD\_LOGIC

);

end mux4\_1;

architecture Behavioral of mux4\_1 is

component mux2\_1

port( A,B : in STD\_LOGIC;

S : in STD\_LOGIC;

Z : out STD\_LOGIC);

end component;

signal temp1, temp2 : std\_logic;

begin

x1 : mux2\_1 port map(A,B,S0,temp1);

x2 : mux2\_1 port map(C,D,S1,temp2);

z1 : mux2\_1 port map(temp1,temp2,S1,Z);

end Behavioral;

view source

print?

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity mux2_1 is
```

```
port(A,B : in STD_LOGIC;
```

```
S: in STD_LOGIC;
```

```
Z: out STD_LOGIC);
```

```
end mux2_1;
```

```
architecture Behavioral of mux2_1 is
```

```
begin
```

```
process (A,B,S) is
```

```
begin
```

```
if (S = '0') then
```

```
Z <= A;
```

```
else
```


```
Z <= B;
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```
 
## VHDL Code of 4:1 Mux using Different Modeling Styles :



### -- Behavioral Modeling of 4:1 mux

```
library ieee;
use ieee.std_logic_1164.all;
entity MUX4_1 is
port ( Sel : in std_logic_vector(1 downto 0);
      A, B, C, D : in std_logic;
      Y : out std_logic );
end MUX4_1;
architecture behavior of MUX4_1 is
begin
process (Sel, A, B, C, D)
begin
if (Sel = "00") then
Y<= A;
elsif (Sel = "01") then
Y<= B;
elsif (Sel = "10") then
Y<= C;
else
Y<= D;
end if;
end process;
end behavior;
```

**-- Structural modeling of 4:1 mux**

**library** ieee;

**use** ieee.std\_logic\_1164.all;

**entity** MUX4\_1 **is**

**port** ( Sel0,Sel1 : **in** std\_logic;

A, B, C, D : **in** std\_logic;

Y : **out** std\_logic );

**end** MUX4\_1;

**architecture** structural of MUX4\_1 **is**

**component** inv

**port** (pin : **in** std\_logic;

pout :**out** std\_logic);

**end component;**

**component** and3

**port** (a0,a1,a2: **in** std\_logic;

aout:**out** std\_logic);

**end component;**

**component** or4

**port** (r0,r1,r2,r3:**in** std\_logic;

rout:**out** std\_logic);

**end component;**

**signal** selbar0,selbar1,t1,t2,t3,t4: std\_logic;

**begin**

INV0: inv **port map** (Sel0, selbar1);

INV1: inv **port map** (Sel1, selbar1);

A1: and3 **port map** (A, selbar0, selbar1, t1);

A2: and3 **port map** (B, Sel0, selbar1, t2);

A3: and3 **port map** (C, selbar0, Sel1, t2);

A4: and3 **port map** (D, Sel0, Sel1, t4);

O1: or4 port map (t1, t2, t3, t4, Y);

**end** structural;

-- Dataflow modeling of 4:1 mux

architecture dataflow of MUX4\_1 is

signal selbar0,selbar1,t1,t2,t3,t4: std\_logic;

begin

selbar0<=not sel0;

selbar1<=not sel1;

t1<=A and selbar0 and selbar1;

t2<=B and sel0 and selbar1;

t3<=C and selbar0 and sel1;

t4<=D and sel0 and sel1;

Y<= t1 or t2 or t3 or t4;

end dataflow;



## Code for 16x1 mux

```
Library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity kanhe_16x1mux is
port(a:in std_logic_vector(15 downto 0);
  s: in std_logic_vector(3 downto 0);
  Z:out std_logic);
End kanhe_16x1mux;

Architecture kanhe_16x1mux1 of kanhe_16x1mux is
signal z1,z2,z3,z4:std_logic;

component kanhe_4x1mux is
port(a,b,c,d,s0,s1:in std_logic;
  Q:out std_logic);

End component;

Begin
M1: kanhe_4x1mux port map(a(0),a(1),a(2),a(3),s(0),s(1),z1);
m2: kanhe_4x1mux port map(a(4),a(5),a(6),a(7),s(0),s(1),z2);
m3: kanhe_4x1mux port map(a(8),a(9),a(10),a(11),s(0),s(1),z3);
m4: kanhe_4x1mux port map(a(12),a(13),a(14),a(15),s(0),s(1),z4);
m5: kanhe_4x1mux port map(z1,z2,z3,z4,s(2),s(3),z);

End kanhe_16x1mux1;
```

vhdl code for 16:1 mux using 8:1 :

```
library IEEE;
```

```
entity mux16using8 is
```

```
    port(d:in bit_vector(15 downto 0);
```

```
          s:in bit_vector(3 downto 0);
```

```
          e:in bit;
```

```
          y:out bit);
```

```
end mux16using8;
```

```
architecture Behavioral of mux16using8 is
```

```
    component mux8 is
```

```
        port(d:in bit_vector(7 downto 0);
```

```
              e:in bit;
```

```
              s:in bit_vector(2 downto 0);
```

```
              y:out bit);
```

```
    end component;
```

```
    component mux2 is
```

```
        port ( d:in bit_vector(1 downto 0);
```

```
              e,s:in bit;
```

```
              y:out bit);
```

```
    end component;
```

```
    signal m:bit_vector(1 downto 0);
```

```
begin
```

```
    m1:mux8 port map(d(7 downto 0),e,s(2 downto 0),m(0));
```

```
    m2:mux8 port map(d(15 downto 8),e,s(2 downto 0),m(1));
```

```
    m3:mux2 port map(m,e,s(3),y);
```

```
end Behavioral;
```

## Multiplexer using case when

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY MUX8_1 IS
PORT (A:IN STD_LOGIC_VECTOR ( DOWNTO 0));
      B:IN STD_LOGIC_VECTOR ( DOWNTO 0);
      C:IN STD_LOGIC_VECTOR ( DOWNTO 0);
      D:IN STD_LOGIC_VECTOR ( DOWNTO 0);
      E:IN STD_LOGIC_VECTOR ( DOWNTO 0);
      F:IN STD_LOGIC_VECTOR ( DOWNTO 0);
      G:IN STD_LOGIC_VECTOR ( DOWNTO 0);
      SEL:IN STD_LOGIC_VECTOR ( DOWNTO 0); DOUT:OUT STD_LOGIC_VECTOR ( DOWNTO 0));
END MUX8_1;

ARCHITECTURE BEH123 OF MUX8_1 IS
BEGIN
PROCESS (A,B,C,D,E,F,G,SEL)
BEGIN
CASE SEL IS
WHEN "000" => DOUT<=A;
WHEN "001" => DOUT<=B;
WHEN "010" => DOUT<=C;
WHEN "011" => DOUT<=D;
WHEN "100" => DOUT<=E;
WHEN "101" => DOUT<=F;
WHEN "110" => DOUT<=G;
WHEN OTHERS=> DOUT<=A;
END CASE;
END PROCESS;
END BEH123;
```

vhdl code for 16:1 mux using 4:1 :

```
Library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
```

```
entity kanhe_4x1mux is
port(a,b,c,d : in std_logic;
S0,s1 : in std_logic;
q : out std_logic);
end kanhe_4x1mux;
```

```
Architecture kanhe_4x1mux1 of kanhe_4x1mux is
Begin
Process(a,b,c,d,s0,s1)
Begin
```

```
If s0='0' and s1='0' then q <= a;
Elsif s0='1' and s1='0' then q <= b;
elsif s0='0' and s1='1' then q <= c;
else q <=d;
end if;
End process;
End kanhe_4x1mux1;
```